


$$U_{OUT} = 1.25 \times \left[1 + \frac{R_B}{R_A} \right] = 1.25 + I_0 \times R_B$$

$$I_0 = \frac{1.25}{R_A} \quad R_B = \frac{U_{OUT \text{ MAX}} - 1.25}{I_0}$$

$$R_{B1} = \frac{U_{OUT1} - 1.25}{I_0} \quad R_{B1} = R_C // R_B = \frac{R_B \times R_C}{R_B + R_C}$$

$$R_C = \frac{R_B \times R_{B1}}{R_B - R_{B1}} \quad U_{OUT1} = 1.25 + I_0 \times R_{B1}$$

WILLEM 4.1, (WILLEM 4.0)

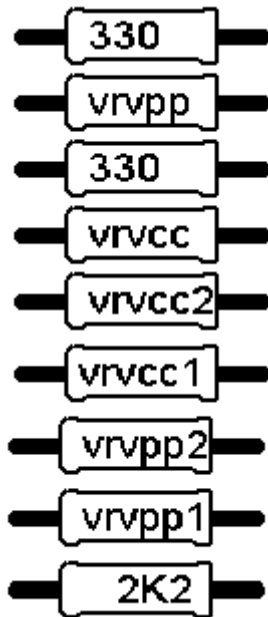

(10k W4.0)

- 324 (orange3, red2, yellow4,black0), schematic R4, (Vpp, RA)
- 6490 (blue6, yellow4, white9, brown1), vrvpp, schematic R3, (Vpp, RB)
- 324 (orange3, red2, yellow4,black0), schematic R2, (Vcc, RA)
- 1240 (brown 1, red2, yellow4, brown1), vrvcc, schematic R1, (Vcc, RB)
- 910 (white9,brown1, black0, black0), vrvcc2, schematic R8, SW1/4, (Vcc, RC2)
- 4300 (yellow 4,orange3, black0,brown1), vrvcc1, schematic R7,SW1/3, (Vcc,RC1)
- 26100 (red2, blue6, brown1, red2), vrvpp2, schematic R6, SW1/1, (Vpp, RC2)
- 5620 (green5, blue6, red2, brown1), vrvpp1, schematic R5, SW1/2, (Vpp, RC1)
- 2k2 (10k W4.0)

Vpp

$$I_0 = 1.25 / R_A = 1.25 / 324 = 3.858 \text{ mA}$$

$$U_{\text{out}} = 1.25 + I_0 \cdot R_B = 1.25 + 0.003858 \cdot 6490 = 26.29 \text{ V}$$

$$R_{B1} = R_B // R_{C1} = (R_B \cdot R_{C1}) / (R_B + R_{C1}) = 6490 \cdot 5620 / (6490 + 5620) = 3012 \text{ Ohm}$$

$$U_{\text{out1}} = 1.25 + I_0 \cdot R_{B1} = 1.25 + 0.003858 \cdot 3012 = 12.87 \text{ V}$$

$$R_{B2} = R_B // R_{C2} = (R_B \cdot R_{C2}) / (R_B + R_{C2}) = 6490 \cdot 26100 / (6490 + 26100) = 5198 \text{ Ohm}$$

$$U_{\text{out2}} = 1.25 + I_0 \cdot R_{B2} = 1.25 + 0.003858 \cdot 5198 = 21.30 \text{ V}$$

Vcc

$$I_0 = 1.25 / R_A = 1.25 / 324 = 3.858 \text{ mA}$$

$$U_{\text{out}} = 1.25 + I_0 \cdot R_B = 1.25 + 0.003858 \cdot 1240 = 6.03 \text{ V}$$

$$R_{B1} = R_B // R_{C1} = (R_B \cdot R_{C1}) / (R_B + R_{C1}) = 1240 \cdot 4300 / (1240 + 4300) = 962 \text{ Ohm}$$

$$U_{\text{out1}} = 1.25 + I_0 \cdot R_{B1} = 1.25 + 0.003858 \cdot 962 = 4.96 \text{ V}$$

$$R_{B2} = R_B // R_{C2} = (R_B \cdot R_{C2}) / (R_B + R_{C2}) = 1240 \cdot 910 / (1240 + 910) = 525 \text{ Ohm}$$

$$U_{\text{out2}} = 1.25 + I_0 \cdot R_{B1} = 1.25 + 0.003858 \cdot 525 = 3.28 \text{ V}$$

Actual voltages (sample W4.1 measured)


26.44V (SW1/1 OFF, SW1/2 OFF), 21.42V (SW1/1 ON, SW1/2 OFF),

12.93V (SW1/1 OFF, SW1/2 ON)

6.05V (SW1/3 OFF, SW1/4 OFF), 4.97V (SW1/3 ON, SW1/4 OFF),

3.27V (SW1/3 OFF, SW1/4 ON)

WILLEM 4.0 (old version, sample)

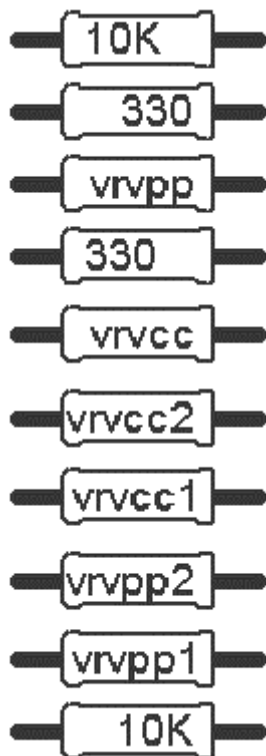

10k

332 (orange3, orange3, red2, black0), schematic R4, (Vpp, RA)

N/C (omitted), vrvpp, schematic R3, (Vpp, RB)

332 (orange3, orange3, red2, black0), schematic R2, (Vcc, RA)

1240 (brown 1, red2, yellow4, brown1), vrvcc, schematic R1, (Vcc, RB)

910 (white9, brown1, black0, black0), vrvcc2, schematic R8, SW1/4, (Vcc, RC2)

4320 (yellow 4, orange3, red2, brown1), vrvcc1, schematic R7, SW1/3, (Vcc, RC1)

5360 (green5, orange3, blue6, red2), vrvpp2, schematic R6, SW1/1, (Vpp, RC2)

3010 (orange3, black0, brown1, brown1), vrvpp1, schematic R5, SW1/2, (Vpp, RC1)

10k

Vpp

$$I_0 = 1.25 / R_A = 1.25 / 332 = 3.765 \text{ mA}$$

RB = high impedance, Uout ~ Uin

$$U_{out1} = 1.25 + I_0 \cdot R_{C1} = 1.25 + 0.003765 \cdot 3010 = 12.58 \text{ V}$$

$$U_{out2} = 1.25 + I_0 \cdot R_{C2} = 1.25 + 0.003765 \cdot 5360 = 21.43 \text{ V}$$

Vcc

$$I_0 = 1.25 / R_A = 1.25 / 332 = 3.765 \text{ mA}$$

$$U_{out \text{ max}} = 1.25 + I_0 \cdot R_B = 1.25 + 0.003765 \cdot 1240 = 5.92 \text{ V}$$

$$R_{B1} = R_B // R_{C1} = (R_B \cdot R_{C1}) / (R_B + R_{C1}) = 1240 \cdot 4320 / (1240 + 4320) = 963 \text{ Ohm}$$

$$U_{out1} = 1.25 + I_0 \cdot R_{B1} = 1.25 + 0.003765 \cdot 963 = 4.88 \text{ V}$$

$$R_{B2} = R_B // R_{C2} = (R_B \cdot R_{C2}) / (R_B + R_{C2}) = 1240 \cdot 910 / (1240 + 910) = 525 \text{ Ohm}$$

$$U_{out2} = 1.25 + I_0 \cdot R_{B2} = 1.25 + 0.003765 \cdot 525 = 3.23 \text{ V}$$

Actual voltages (sample measured)


Uout ~ Uin (SW1/1 OFF, SW1/2 OFF), **DON'T USE OPTION WITHOUT vrvpp !**

21.67V (SW1/1 ON, SW1/2 OFF), 12.71V (SW1/1 OFF, SW1/2 ON)

6.01V (SW1/3 OFF, SW1/4 OFF), 4.95V (SW1/3 ON, SW1/4 OFF),

3.27V (SW1/3 OFF, SW1/4 ON)

WILLEM 4.5

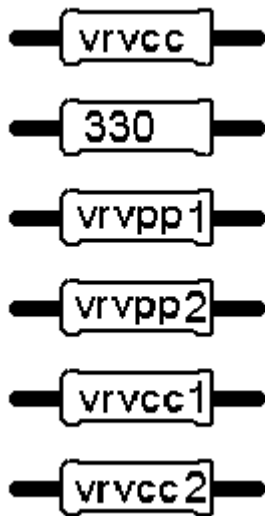

1240 (brown 1, red2, yellow4, brown1), vrvcc, schematic R1, (Vcc, RB)
324 (orange3, red2, yellow4,black0), schematic R2, (Vcc, RA)
750 (violet7, green5, black0,black0), vrvpp1, schematic R5, SW1/2, (Vcc, RC1)
511 (green5,brown1, brown1, black0), vrvpp2, schematic R6, SW1/1, (Vcc, RC2)
910 (white9,brown1, black0, black0), vrvcc1, schematic R7, SW1/3, (Vcc, RC3)
4300 (yellow 4,orange3, black0,brown1), vrvcc2, schematic R8,SW1/4, (Vcc,RC4)

Vcc

$$I_0 = 1.25 / R_A = 1.25 / 324 = 3.858 \text{ mA}$$

$$U_{\text{out}} = 1.25 + I_0 \cdot R_B = 1.25 + 0.003858 \cdot 1240 = 6.03 \text{ V}$$

$$R_{B1} = R_B // R_{C1} = (R_B \cdot R_{C1}) / (R_B + R_{C1}) = 1240 \cdot 750 / (1240 + 750) = 467 \text{ Ohm}$$

$$U_{\text{out1}} = 1.25 + I_0 \cdot R_{B1} = 1.25 + 0.003858 \cdot 467 = 3.05 \text{ V}$$

$$R_{B2} = R_B // R_{C2} = (R_B \cdot R_{C2}) / (R_B + R_{C2}) = 1240 \cdot 511 / (1240 + 511) = 362 \text{ Ohm}$$

$$U_{\text{out2}} = 1.25 + I_0 \cdot R_{B1} = 1.25 + 0.003858 \cdot 362 = 2.65 \text{ V}$$

$$R_{B3} = R_B // R_{C3} = (R_B \cdot R_{C3}) / (R_B + R_{C3}) = 1240 \cdot 910 / (1240 + 910) = 525 \text{ Ohm}$$

$$U_{\text{out1}} = 1.25 + I_0 \cdot R_{B1} = 1.25 + 0.003858 \cdot 525 = 3.28 \text{ V}$$

$$R_{B4} = R_B // R_{C4} = (R_B \cdot R_{C4}) / (R_B + R_{C4}) = 1240 \cdot 4300 / (1240 + 4300) = 962 \text{ Ohm}$$

$$U_{\text{out1}} = 1.25 + I_0 \cdot R_{B1} = 1.25 + 0.003858 \cdot 962 = 4.96 \text{ V}$$

Actual voltages (sample measured)

6.05V (SW1/1 OFF, SW1/2 OFF, SW1/3 OFF, SW1/4 OFF),

4.97V (SW1/1 OFF, SW1/2 OFF, SW1/3 OFF, SW1/4 ON),

3.26V (SW1/1 OFF, SW1/2 OFF, SW1/3 ON, SW1/4 OFF)

3.05V (SW1/1 OFF, SW1/2 ON, SW1/3 OFF, SW1/4 OFF),

2.64V (SW1/1 ON, SW1/2 OFF, SW1/3 OFF, SW1/4 OFF)

Create own resistor set for Willem 4.1

Selected Vpp= 26.0, 21.5, 12.8 V

RA= R4 =324 (original precise resistor)

Io=1.25/324=0.003858 A

Uout max=Vpp=26.0V

RB= (Uout max-1.25)/Io = (26.0-1.25)/0.003858=6415 Ohm

Place generic resistors vrvpp=R3= 6k2+220 (6420) , check output voltage.

Adjust 220 Ohm if required (200...240) to have closest 26.0V voltage.

Calculate real summar resistor value from measured Uout, RB=(Uout-1.25)/Io, (6420)

Uout2=Vpp=21.5V

RB2= (Uout2-1.25)/Io = (21.5-1.25)/0.003858=5249 Ohm

RC2= RB* RB2 / (RB-RB2) = 6420*5249 / (6420-5249)=29764 Ohm

Place generic resistors vrvpp2=R6= 27k+2k7 .

SW1/1 ON, SW1/2 OFF, check output voltage.

Adjust 2k7 if required (2k...3k3) to have closest 21.5V voltage.

Uout1=Vpp=12.8V

RB1= (Uout1-1.25)/Io = (12.8-1.25)/0.003858=2994 Ohm

RC1= RB* RB1 / (RB-RB1) = 6420*2994 / (6420-2994)=5610 Ohm

Place generic resistors vrvpp1=R5= 5k1+510 .

SW1/1 OFF, SW1/2 ON, check output voltage.

Adjust 510 if required (470...560) to have closest 12.8 voltage.

Selected Vcc= 5.9, 5.05, 3.3 V

RA= R2 =324 (original precise resistor)

Io=1.25/324=0.003858 A

Uout max=Vcc=6.0V

RB= (Uout max-1.25)/Io = (6.0-1.25)/0.003858=1231 Ohm

Place generic resistors vrvcc=R1= 1k1+130 (1230) , check output voltage.

Adjust 130 Ohm if required (100...150) to have closest 6.0V voltage.

Calculate real summar resistor value from measured Uout, RB=(Uout-1.25)/Io, (1230)

Uout1=Vcc=5.05V

RB1= (Uout1-1.25)/Io = (5.05-1.25)/0.003858=985 Ohm

RC1= RB* RB1 / (RB-RB1) = 1230*985 / (1230-985)= 4945 Ohm

Place generic resistors vrvcc1=R7= 4k7+240

SW1/3 ON, SW1/4 OFF, check output voltage.

Adjust 240 if required (200...300) to have closest 5.05 V voltage.

Uout2=Vcc=3.3V

RB2= (Uout2-1.25)/Io = (3.3-1.25)/0.003858=531 Ohm

RC2= RB* RB2 / (RB-RB2) = 1230*531 / (1230-531)= 934 Ohm

Place generic resistors vrvcc2=R8= 820+110

SW1/3 OFF, SW1/4 ON, check output voltage.

Adjust 110 if required (91...130) to have closest 3.3 V voltage.

All Vcc voltages are a bit too low (for example Willem 4.0 with R2=332)

Existing results

$$R_A=R_2=332 \text{ Ohm}$$

$$I_o=1.25/332=0.003765 \text{ A}$$

$$R_{B1}=R_B//R_{C1}=(R_B \cdot R_{C1})/(R_B+R_{C1})=1240 \cdot 4320/(1240+4320)=963 \text{ Ohm}$$

$$U_{out1}=1.25+I_o \cdot R_{B1}=1.25+0.003765 \cdot 963=4.88 \text{ V}$$

Increase Uout1 from 4.88V to 5.0V

$$I_{o1}=(U_{out1}-1.25)/R_{B1}=(5.0-1.25)/963=0.003894 \text{ A}$$

$$R_{A1}=1.25/I_{o1}=1.25/0.003894=321 \text{ Ohm}$$

$$R_A^*=332 \cdot 321 / (332-321)=9688 \text{ Ohm}$$

Place 10k parallel to $R_A=R_2$ and check voltages 5.0 / 6.0 / 3.3 V

$$R_{A1}=10000 \cdot 332 / (10000+332)=321 \text{ Ohm}$$

$$I_o=1.25/321=0.003894 \text{ A}$$

$$U_{out \text{ max}}=1.25+I_o \cdot R_B=1.25+0.003894 \cdot 1240=6.08 \text{ V (ex 5.92V)}$$

$$U_{out1}=1.25+I_o \cdot R_{B1}=1.25+0.003894 \cdot 963=5.00 \text{ V (ex 4.88V)}$$

$$U_{out2}=1.25+I_o \cdot R_{B2}=1.25+0.003894 \cdot 525=3.29 \text{ V (ex 3.23V)}$$

Adjust particular Vcc or Vpp

Adjusted $U_{out \text{ max}}$ ($V_{pp} \sim 26 \text{ V}$, $V_{cc} \sim 6.0 \text{ V}$) with R_A (324, 332 or parallel resistor) or R_B (v_{rvpp} , v_{rvcc}), all other resistors (v_{rvpp1} , v_{rvpp2} , v_{rvcc1} , v_{rvcc2}) should be recalculated !

Any other voltage ($V_{cc}/V_{pp} - U_{out1}$, U_{out2}) can be adjusted individually .

For example Willem 4.0 with $R_2=332$, $R_A=R_2=332 \text{ Ohm}$

$$I_o=1.25/332=0.003765 \text{ A}$$

$$R_{B1}=R_B//R_{C1}=(R_B \cdot R_{C1})/(R_B+R_{C1})=1240 \cdot 4320/(1240+4320)=963 \text{ Ohm}$$

$$U_{out1}=1.25+I_o \cdot R_{B1}=1.25+0.003765 \cdot 963=4.88 \text{ V}$$

Adjust Uout1= 4.88V >> 5.0V

$$R_{B1}=(U_{out1}-1.25)/I_o=(5.0-1.25)/0.003765=996 \text{ Ohm}$$

$$R_{C1}=R_B \cdot R_{B1} / (R_B-R_{B1})=1240 \cdot 996 / (1240-996)=5061 \text{ Ohm}$$

Replace $v_{rvcc1}=R_7$ from 4320 to 4k7+360 and check voltage.


Adjust 360 if required (300...430) to have closest 5.0 V voltage.

Add variable Vcc option , for example to get Vcc=4.5V (eprom erase verify)

Willem 4.1 modification described in picture:

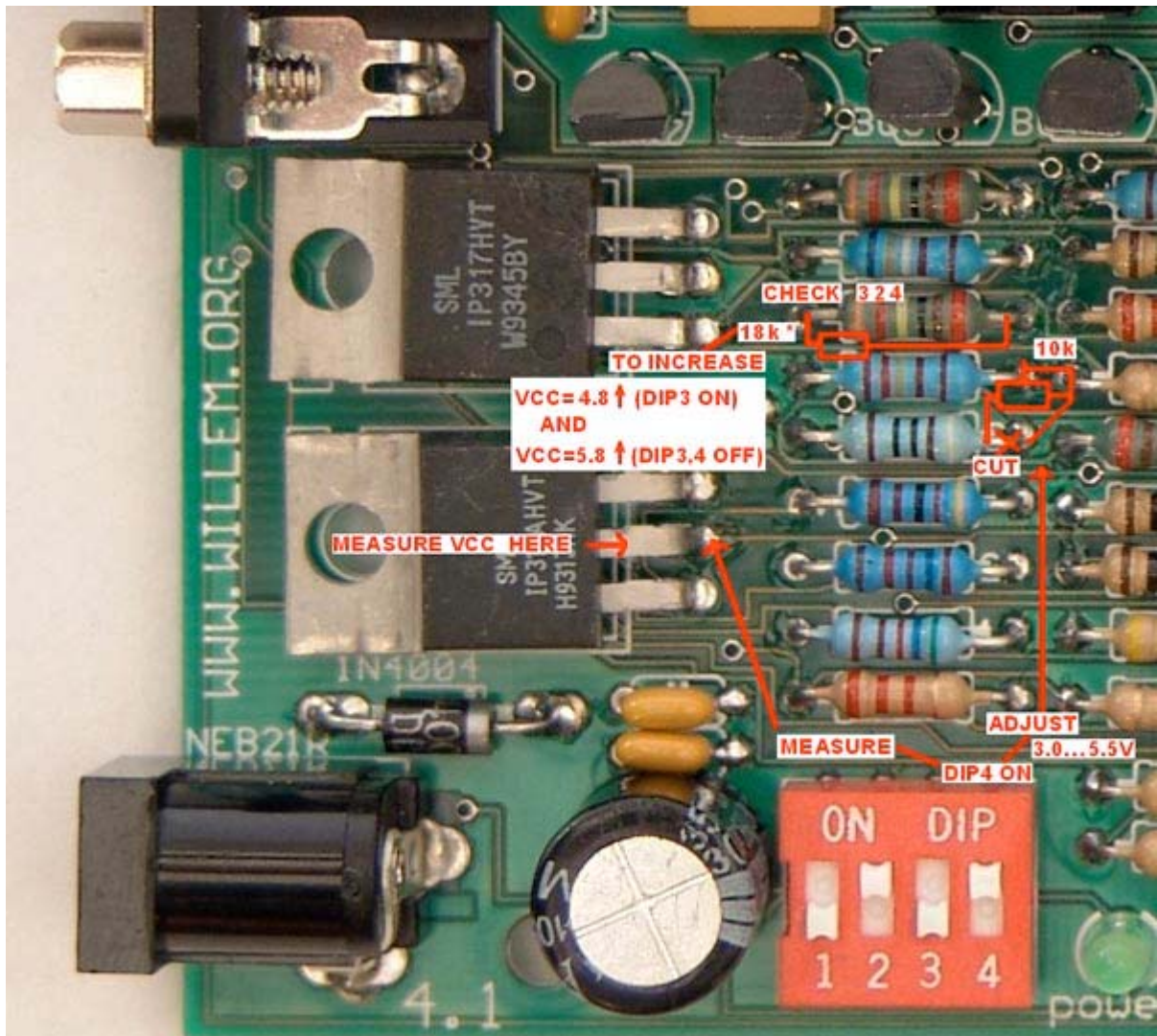- 1) check Vcc related R2=324
- 2) add 18k parallel R2 to increase all Vcc voltages (if R2=332 used)
- 3) cut resistor rvcc2=R8 910 and add serial variable resistor 10k
SW1/3 OFF, SW1/4 ON

Fixed voltage Uout2 ~3.3V comes variable in range 3.3...5.5V with variable resistor now.



Add Vpp=14V support for electrically erasable eproms W27E/C256....040

Existing Willem programmers 4.0/4.1 don't support Vpp=14V required to erase electrically erasable eproms W27E256..040 (Jp6/2-3 SF erase)

Vpp=14.7V+-0.5V required, 0.7V drop on diod D9.

Selected modification:

SW1/1 OFF, SW1/2 OFF , Vpp=25V;

SW1/1 ON, SW1/2 OFF , Vpp=21V;

SW1/1 OFF, SW1/2 ON , Vpp=14.7V;

SW1/1 ON, SW1/2 ON , Vpp=12.8V

Change resistor vrvpp1= R5 from 5620 to 6k8+470 (7270)

Check voltages in both ranges Vpp=14.7 and Vpp=12.8

Adjust resistor 470 if required (390....560) to keep both voltages in acceptable range.

Vpp

$$I_0 = 1.25 / R_A = 1.25 / 324 = 3.858 \text{ mA}$$

$$U_{\text{out}} = 1.25 + I_0 \cdot R_B = 1.25 + 0.003858 \cdot 6490 = 26.29 \text{ V}$$

$$R_{B2} = R_B // R_{C2} = (R_B \cdot R_{C2}) / (R_B + R_{C2}) = 6490 \cdot 26100 / (6490 + 26100) = 5198 \text{ Ohm}$$

$$U_{\text{out}2} = 1.25 + I_0 \cdot R_{B2} = 1.25 + 0.003858 \cdot 5198 = 21.30 \text{ V}$$

$$R_{B1} = R_B // R_{C1} = (R_B \cdot R_{C1}) / (R_B + R_{C1}) = 6490 \cdot 7270 / (6490 + 7270) = 3429 \text{ Ohm}$$

$$U_{\text{out}1} = 1.25 + I_0 \cdot R_{B1} = 1.25 + 0.003858 \cdot 3429 = 14.48 \text{ V}$$

$$R_{B3} = R_B // R_{C1} // R_{C2} = (R_{B1} \cdot R_{C2}) / (R_{B1} + R_{C2}) = 3429 \cdot 26100 / (3429 + 26100) = 3031 \text{ Ohm}$$

$$U_{\text{out}3} = 1.25 + I_0 \cdot R_{B3} = 1.25 + 0.003858 \cdot 3031 = 12.94 \text{ V}$$